


W8

12

WIDE BAND VIDEO AMP

Recall f_{-3dB} of OP AMP ≈ 20 Hz

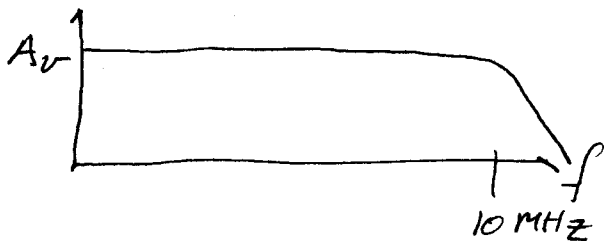VIDEO \Rightarrow flat response out into MHz



* Trade off gain for bandwidth


* Use feedback

- V_i large +, M_3 & M_6 cut-off
 - M_2 & M_7 larger $V_{GS} \Rightarrow$ larger I_D
 - large neg. value I_D
 - ∴ Large I available beyond linear region.
- ~~30 $\frac{eV}{\mu s}$ BJT op amps~~
~~30 V MHz (switch 1 V @ 30 MHz)~~

END CH. 9

WIDEBAND VIDEO Amps

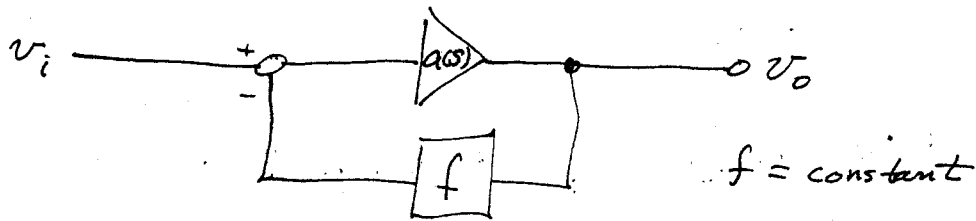- USE negative feedback to
 - Op Amps \rightarrow high open loop gain 10^5 (100dB) - 10^6 (120dB) at low f.
 - Sacrifice f response. $f_{-3dB} = 5$ Hz
 - Video amps - flat, wideband gain up to 4-6 MHz TV some apps. 50 MHz
 - Gain-Bandwidth trade-off
 - Use
 - Reduced load resistance for stages of amp
 - negative feedback
- $A_v = G_m R_o$



$a(s) = \frac{a_0}{1 - \frac{s}{p_1}}$ single pole
 $a_0 = \text{low } f \text{ gain.}$

Overall gain: $A(s) = \frac{v_o}{v_i} = \frac{a(s)}{1 + fa(s)}$


$$A(s) = \frac{\frac{a_o}{1-s/p_1}}{1 + \frac{a_o f}{1-s/p_1}} = \frac{a_o}{1 - \frac{s}{p_1} + a_o f}$$

$$= \underbrace{\frac{a_o}{1 + a_o f}}_{A_o} \frac{1}{1 - \frac{s}{p_1(1+a_o f)}}$$

Low freq. gain $A_o = \frac{a_o}{1 + a_o f}$

New pole $P_1 = p_1(1 + a_o f)$

f_{-3dB} increased by $(1 + a_o f)$

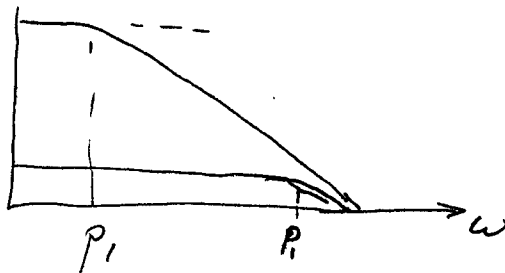

$(\text{Gain} \cdot \text{Bandwidth}) (\omega=0) = \text{const.}$

Feedback is internal - reducing A_{vo} of diff amp.