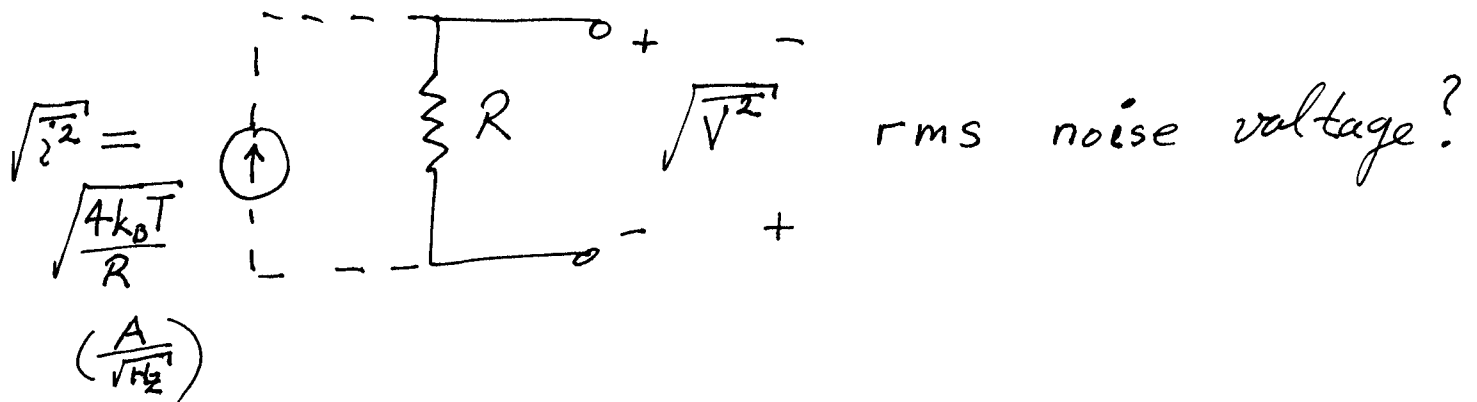


CH. 7 NOISE in resistors (Sec. 7.3)

Thermal or Johnson noise


- Random motion of electrons due to thermal effects.
- Model with a parallel current source



$$\sqrt{i^2} = \sqrt{\frac{4k_B T}{R}} \cdot \sqrt{B} \quad B = \text{bandwidth in Hz.}$$

Leave out B until end of calculation.
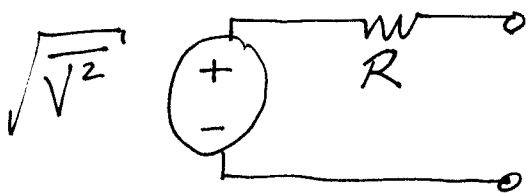
$$\sqrt{V^2} = \sqrt{i^2} R = \sqrt{4k_B T R} \left(\frac{V}{\sqrt{Hz}} \right)$$



$$\text{TOTAL RMS Noise Voltage} = \sqrt{V^2} \sqrt{B}$$

NOISE Analysis

1.2

1. Add RMS noise sources to circuit
2. Determine RMS circuit output noise from each component using superposition
3. Square each ^{output} noise component
4. Add together

OUTPUT NOISE


5. Integrate over bandwidth
6. Take $\sqrt{\quad}$ of result

Input Referred Noise

5. Divide sum in (4) by $|H(j\omega)|^2$

$$= \left| \frac{V_o}{V_{in}} \right|^2$$


6. Integrate over bandwidth
7. $\sqrt{\quad}$

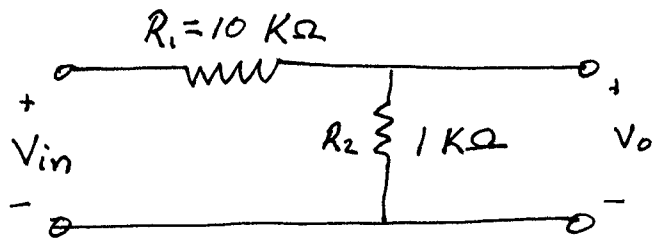Example

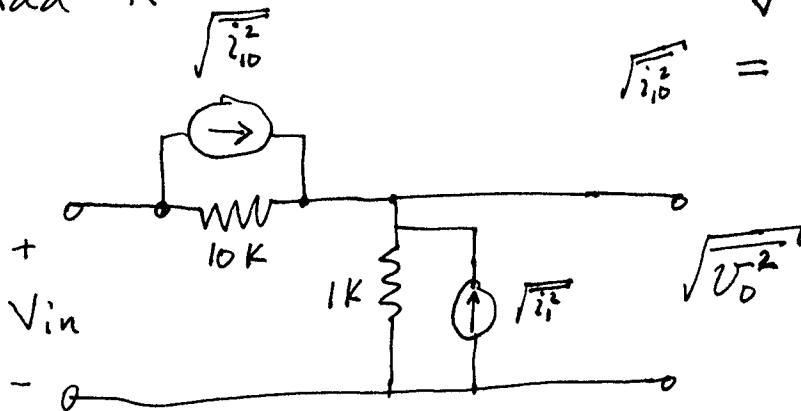(1) Add RMS noise sources $\sqrt{i_{10}^2} = \sqrt{\frac{4 \cdot 0.026 \cdot 1.602e-19}{10^4}}$

$$\sqrt{i_{10}^2} = 1.29e-12 \frac{A}{\sqrt{Hz}}$$

$$\sqrt{i_1^2} = 4.08e-12 \frac{A}{\sqrt{Hz}}$$




(2) Superposition

"Kill" all sources but one of interest

i.e. short Voltage sources

Open Current sources

⇒ (a) Short V_{in}

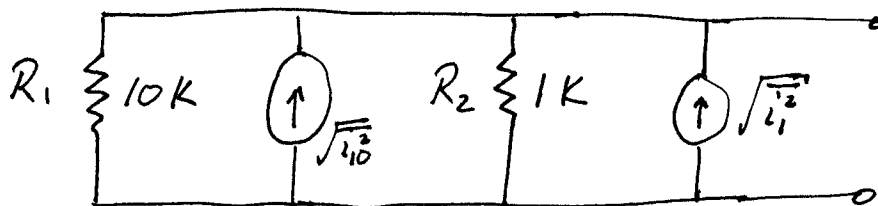

(b) Open $\sqrt{i_1^2}$

$$\sqrt{v_{10}^2} = \sqrt{i_{10}^2} R_1 \parallel R_2 = \sqrt{i_{10}^2} \frac{10}{11} \text{ k}\Omega$$

$$\sqrt{v_{10}^2} = 1.17 \frac{\text{nV}}{\sqrt{\text{Hz}}}$$

(c) Open $\sqrt{i_{10}^2}$ (close $\sqrt{i_1^2}$)

$$\sqrt{v_1^2} = \sqrt{i_1^2} R_1 \parallel R_2 = 3.71 \frac{\text{nV}}{\sqrt{\text{Hz}}}$$

(3) Square each output noise component
 (4) Add together
 ~~$\sqrt{v_0^2}$~~

$$\overline{v_0^2} = \overline{v_{10}^2} + \overline{v_1^2} = 1.5133e-17 \frac{\text{V}^2}{\text{Hz}}$$

Output Noise

(5) Integrate over Bandwidth (1000 Hz)


$$\overline{v_0^2} \cdot 1000 \text{ Hz} = 1.5133e-14 \text{ V}^2$$

(6) Take $\sqrt{\quad}$

$$\sqrt{\overline{v_0^2}} = 1.23e-7 \text{ V} = 0.123 \mu\text{V}$$

$$\boxed{\sqrt{\overline{v_0^2}} = 123 \text{ nV}}$$

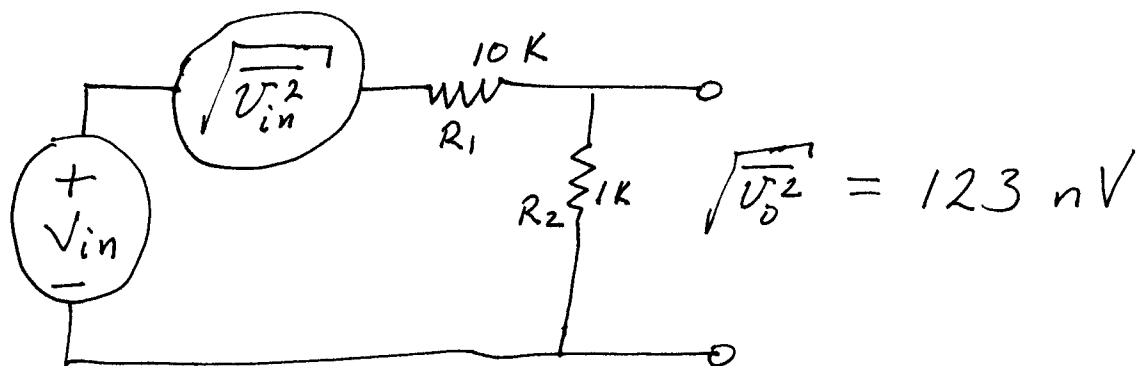Effective Input Noise (Input referred noise)




What noise source at input will generate 123 nV noise at output?

$$\sqrt{V_{in}^2} \frac{1\text{K}}{1\text{K} + 10\text{K}} = 123\text{ nV}$$


$$\sqrt{V_{in}^2} = 1.35\text{ }\mu\text{V}$$

MODEL Noise with SPICE

• noise statement in netlist pp. 143-4

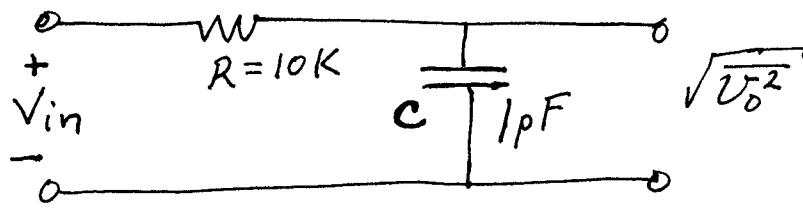Example

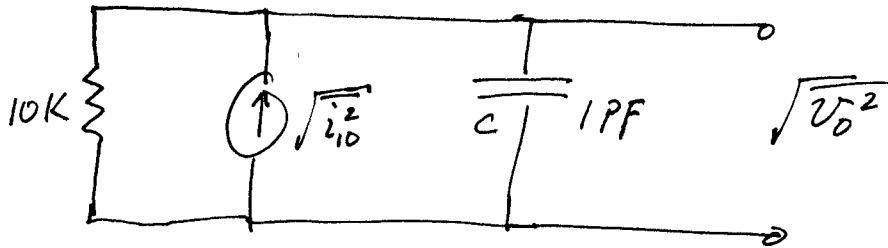(1) & (2) Add Sources + Superposition ("kill" V_{in})



$$\sqrt{i_{10}^2} = 1.29 e^{-12} \frac{A}{\sqrt{Hz}}$$

$$Z = 10 \text{ k}\Omega \parallel 1 \text{ pF} = \frac{R \frac{1}{j\omega C}}{R + \frac{1}{j\omega C}} = \frac{R}{1 + j\omega RC}$$

$$\sqrt{V_o^2} = \sqrt{i_{10}^2} |Z| = \sqrt{i_{10}^2} \frac{R}{\sqrt{1 + \omega^2 R^2 C^2}}$$

$$\sqrt{V_o^2} = \sqrt{i_{10}^2} \frac{R}{\sqrt{1 + (2\pi f RC)^2}}$$

$$(3) \text{ Square: } \overline{v_o^2} = \overline{i_{10}^2} \frac{R^2}{1 + (2\pi f RC)^2}$$

(4) Add all contributions together.

Output Noise

(5) Integrate over f .

$$\int_0^{f_H} df \overline{i_{10}^2} \frac{R^2}{1 + (2\pi f RC)^2}$$

$$u = 2\pi f RC \quad du = 2\pi RC df$$


$$\overline{v_o^2} = \int_0^{2\pi RC f_H} du \frac{R^2}{2\pi RC} \overline{i_{10}^2} \underbrace{\frac{1}{1+u^2}}_{\text{atan}(u)}$$

Let $f_H \rightarrow \infty$

$$\overline{v_o^2} = \frac{\overline{i_{10}^2} R^2}{2\pi RC} \frac{\pi}{2}$$

$$\overline{v_o^2} = \frac{(1.29e-12)^2 (10^4)^2}{4 (10^4) (10^{-12})} = 4.16e-9 \text{ (V}^2\text{)}$$

$$\sqrt{\overline{v_o^2}} = 6.45e-5 \text{ V} = \boxed{64.5 \mu\text{V}}$$

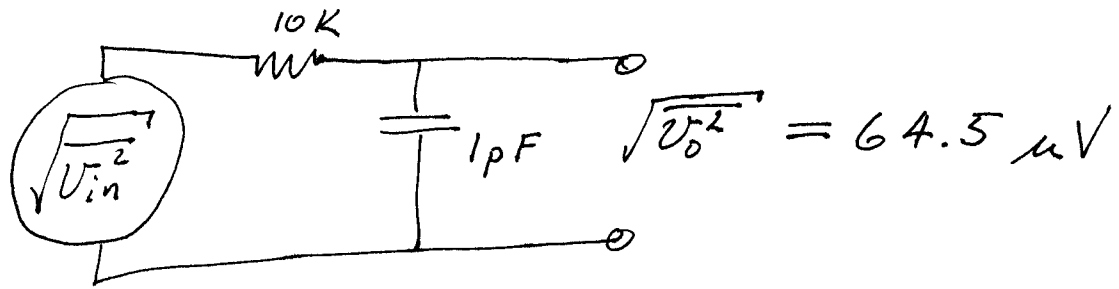Input Noise

(5) Divide sum in (4) by

$$|H(j\omega)|^2 = \left| \frac{V_o}{V_{in}} \right|^2 = |$$

$$V_o = V_i \frac{\frac{1}{j\omega C}}{R + \frac{1}{j\omega C}} = V_i \frac{1}{1 + j\omega RC}$$

$$|H(j\omega)|^2 = \frac{1}{1 + (\omega RC)^2}$$

$$\frac{\overline{V_o^2}}{|H|^2} = \overline{i_{10}^2} \frac{R^2}{1 + (2\pi f RC)^2} (1 + (\omega RC)^2)$$

$$\overline{V_{in}^2} = \overline{i_{10}^2} R^2$$

(6) Integrate over bandwidth

$$\int_0^{f_H} df \overline{i_{10}^2} R^2 = \overline{i_{10}^2} R^2 f_H$$

(7) Take $\sqrt{\quad}$: $\sqrt{\overline{V_{in}^2}} = \sqrt{\overline{i_{10}^2} R^2} \sqrt{f_H}$